

HMK # 11

2a)

D_1	D_0
1	0
0	1
1	1
0	0

Present State	
Q_1	Q_0
0	0
1	0
0	1
1	1

Next State	
Q_1^+	Q_0^+
1	0
0	1
1	1
0	0

if you are asked to design anything you will need to identify design steps.


Sequence of States = 00, 10, 01, 11

$$D_1 = \bar{Q}_1 \cdot \bar{Q}_0 + \bar{Q}_1 \cdot Q_0$$


$$D_0 = Q_1 \cdot \bar{Q}_0 + \bar{Q}_1 \cdot Q_0$$

OUTPUT

is $Q_0 Q_1$

 

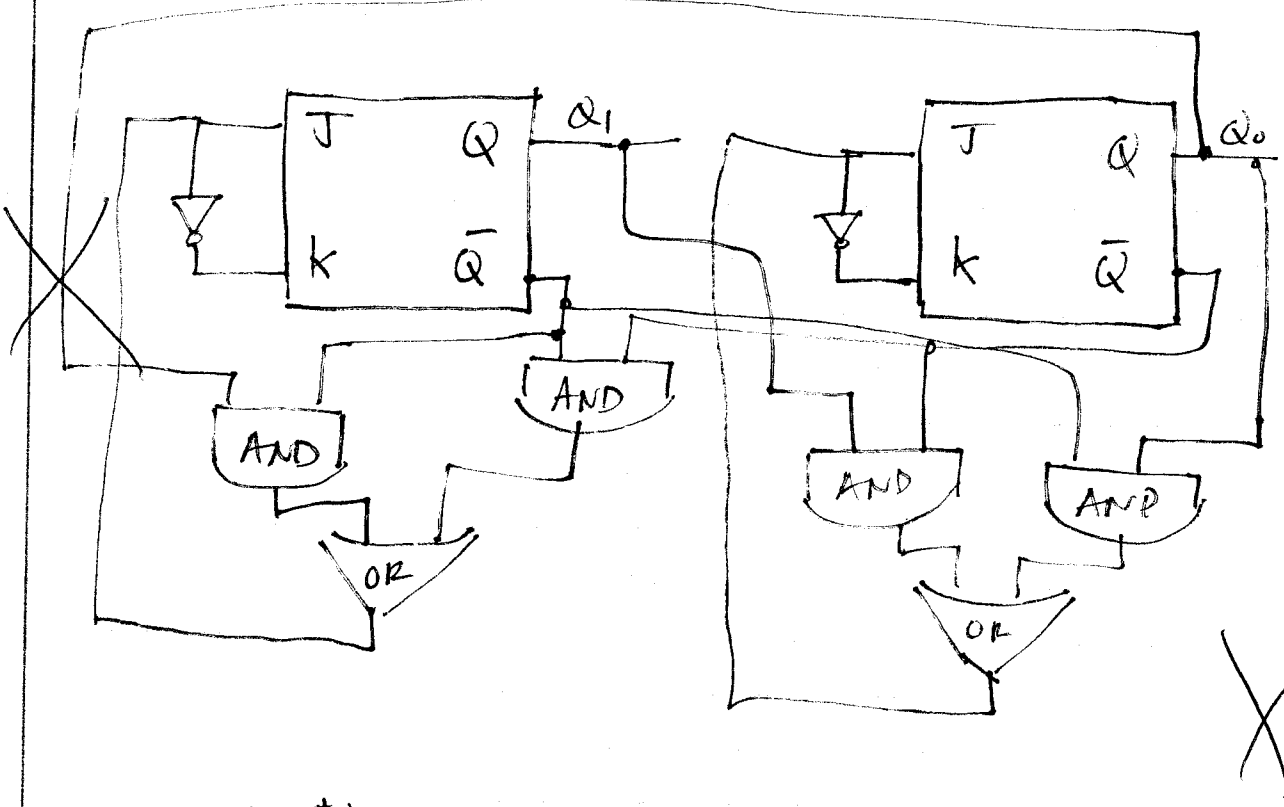2b) By converting JK flip flops to D-flip-flops we can use the last design



IN this problem I expect you to show that you can design a counter with J and k, not adapting the D design.

3a)

step 1

$$D_A = \overline{T \cdot Q_A}$$

$$D_B = \overline{Q_A} \oplus \overline{Q_B}$$

$$D = Q_B + Q_A$$

step 2

T=0

T	D _A	Q _A	$\overline{Q_A}$	Q _A ⁺	D _B	Q _B	$\overline{Q_B}$	Q _B ⁺	D
0	1	0	1	1	0	0	1	0	0
0	1	1	0	1	1	0	1	1	1
0	1	1	0	1	0	1	0	0	1
0	1	1	0	1	1	0	1	1	1

State

Q _A	Q _B
0	0
1	0
1	1
1	0
⋮	

T=1


T	D _A	Q _A	$\overline{Q_A}$	Q _A ⁺	D _B	Q _B	$\overline{Q_B}$	Q _B ⁺	D
1	1	0	1	1	0	0	1	0	0
1	0	1	0	0	1	0	1	1	1
1	1	0	1	1	1	1	0	1	1
1	0	1	0	0	0	1	0	0	1

State

Q _A	Q _B
0	0
1	0
0	1
1	1
0	0
⋮	

State Diagram

step 3

 


3b) X.

D_A	Q_A	\bar{Q}_A	\bar{Q}_A	Q_A^+	D_B	Q_B	\bar{Q}_B	\bar{Q}_B	Q_B^+	J_C	K_C	Q_C	\bar{Q}_C	Q_C^+	J_D	K_D	Q_D	\bar{Q}_D	Q_D^+	State
1	0	1	1	0	0	0	1	0	0	0	0	1	0	1	1	0	1	1	0	0000
0	1	0	0	1	1	0	1	1	1	1	0	1	1	1	1	1	0	0	0	0001
1	0	1	1	1	1	0	1	1	0	1	0	1	0	1	1	1	0	1	1	0110
1	1	0	1	0	0	1	0	0	0	1	1	0	0	0	0	0	1	0	1	1101

1001

State Machine.

 

$$D_A = \overline{Q_D \cdot Q_C}$$

$$D_B = \bar{Q}_A \oplus \bar{Q}_B$$

$$K_C = Q_A / D_A \text{ (Conflict Error)}$$

$$J_D = D_A \oplus Q_D$$


$$K_C = Q_A \text{ (Assumed)}$$

$$K_D = \bar{J}_D$$

J	K	Q_{next}
0	0	0
0	1	0
1	0	1
1	1	1

Analysis: you need to show 3 step process

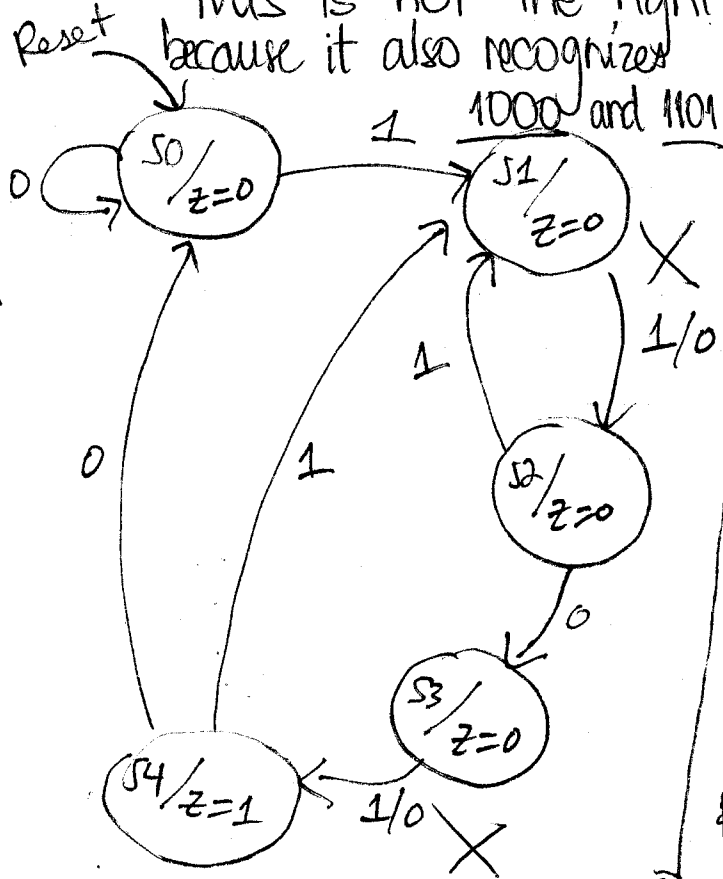4 Word \rightarrow 1100 or 1001
 This is not the right state machine because it also recognizes 1000 and 1101



state machine
 Entity Sequence is
 port (Clock, Reset, w: in std_logic;
 z: out std_logic);
 end sequence

Architecture behavior of
 sequence is
 type state_type is
 (S0, S1, S2, S3, S4);
 signal y: state_type
 begin
 process (Reset, Clock)
 begin

```

if Reset = '1' then y <= S0;
elsif (Clock'Event and Clock = '1') then
  case y is
    when S0 => if w = '0' then y <= S0; else y <= S1; end if;
    when S1 => y <= S2;
    when S2 => if w = '0' then y <= S3; else y <= S1; end if;
    when S3 => y <= S4;
    when S4 => if w = '0' then y <= S0; else y <= S1; end if;
  end case;
end if;
end process;
z <= '1' when (y = S4) else '0';
end behavior;

```

5a) (SIN)

$$D_A = (\overline{Q_E \oplus Q_D}) \cdot (Q_D \oplus Q_C) \cdot Q_B$$

$$D_B = Q_A \quad D_C = Q_B \quad D_D = Q_C \quad D_E = Q_D$$

State shifting

look at the sequence of 1's

D_A	D_B	D_C	D_D	D_E	Q_A	Q_A^+	Q_B	Q_B^+	Q_C	Q_C^+	Q_D	Q_D^+	Q_E	Q_E^+
1	1	1	1	1	0	1	0	1	1	0	1	1	1	1
0	1	1	1	1	0	0	0	0	1	1	1	1	1	1
0	0	1	1	1	0	0	0	0	0	1	1	1	1	1
0	0	0	1	1	0	0	0	0	0	0	1	1	1	1
0	0	0	0	1	0	0	0	0	0	0	0	1	1	1
0	0	0	0	0	0	0	0	0	0	0	0	0	1	1
0	0	0	0	0	0	0	0	0	0	0	0	0	0	1

Assuming all Q's = '1' as initial state

Based on the equation for D_A (SIN) if All Q's = '0' then D_A will never become '1'. Please explain.

This is a cycle shift register.