

HOMEWORK 8 - due **Tuesday**, November 6th at **≤6pm**

1) Feedback (3pts) - to be completed after you finish.

- F1. If you worked on it with classmates and your solutions might be TOO similar, write their names here: _____
- F2. How long did it take you to work on the homework (don't count the reading assignment!)
1h 2h 4h infinite hours
- F3. Do you have suggestions on how to improve it? (ideas for new problems?) Let us know here (and/or use your own homework sheets):

2) CMOS circuit design (20 pts)

Implement a two input XOR gate using PMOS and NMOS transistors.

3) Interfacing gates (30 pts)

(a) Determine the fanout limit when a **Texas Instruments** SN7400 (Quad 2-Input NAND) drives an **ON Semiconductor** SN74LS00 (Quad 2-Input NAND). For the SN74LS00, assume $V_{IN}=2.7$ V when determining I_{IH} , if needed.

(b) Determine the fanout limit when an **ON Semiconductor** SN74LS00 (Quad 2-Input NAND) drives a **Texas Instruments** SN7400 (Quad 2-Input NAND). For the SN74LS00, assume $V_{IN}=2.7$ V when determining I_{IH} , if needed.

4) Power dissipation (27 pts)

For each IC listed below, determine the quiescent power dissipation, dynamic power dissipation and total power dissipation when one gate from each IC drives a capacitive load of $CL = 15$ pF at switching frequencies of 100 kHz, 1 MHz and 10 MHz at $V_{CC} = 5$ V. Assume the gate output is HIGH 3/4 of the time and LOW 1/4 of the time.

- a) ON Semiconductor 74LS283
- b) Philips 74F283
- c) Philips 74HC283

5) Power dissipation again. (20)

For a CMOS inverter, assume that the load capacitance is $C=150$ fF and $V_{cc}=5$ V. The inverter is cycled through the low and high voltage levels at an average rate of $f=75$ MHz.

- (a) Calculate the dynamic power dissipated in the inverter.
- (b) For a chip that contains the equivalent of 450,000 inverters, calculate the total dynamic power dissipated if 15 percent of the gates change values at any given time.

6) Extra credit (10pts: either 10 or 0, adding to a max of 100 as your final grade).

Define a Schmitt-trigger input. In particular, look at the SN74HC7002 (Texas Instruments), (a) identify the main difference between that chip and a non-Schmitt-trigger chip (write a couple of sentences!), (b) draw the symbol that identifies the Schmitt-trigger, and (c) present at least one application where that would be necessary. <http://focus.ti.com/lit/ds/symlink/sn74hc7002.pdf>