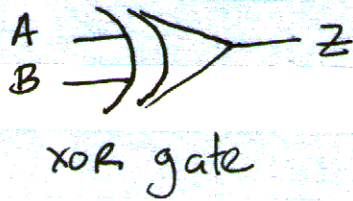



HWK #8

②



| A | B | Z |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

Show how you got from here to here

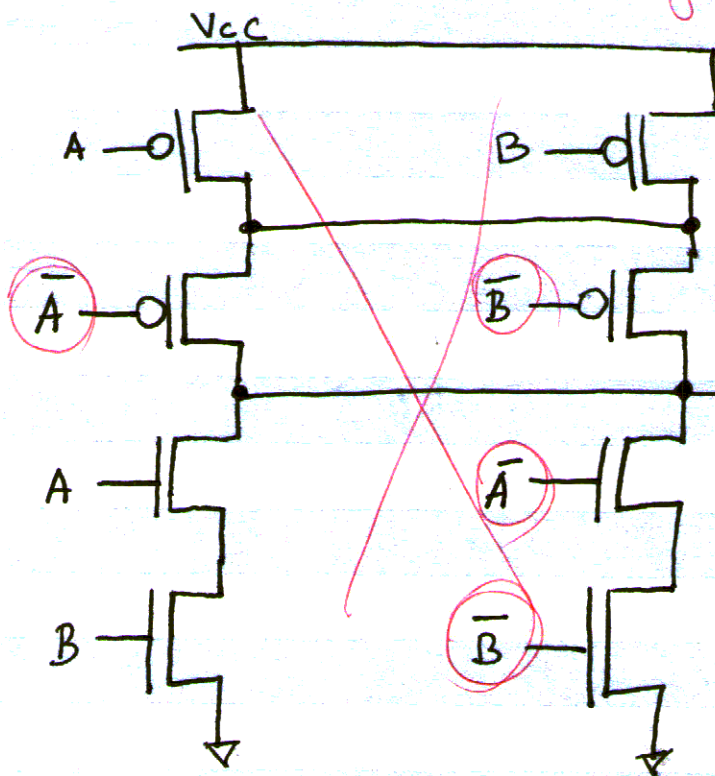

No,

$$Z = \overline{\overline{A} \cdot \overline{B}} + A \cdot B = A \oplus B$$

$$Z = \overline{A}B + A\overline{B}$$

Way to do this:

- ① find Z
- ② Either use NANDs and NORs given in class to implement the circuit, or try the shorthand method discussed in class

(3)

$$\text{DC Fanout} = \min \left(\left| \frac{I_{\text{out high}}}{I_{\text{in high}}} \right|, \left| \frac{I_{\text{out low}}}{I_{\text{in low}}} \right| \right)$$

a) SN7400 drives SN74LS00 \longleftrightarrow $V_{\text{IN}} = 2.7\text{V}$

$$\begin{aligned} \text{Fanout} &= \min \left(\left| \frac{I_{\text{out high}} (\text{SN7400})}{I_{\text{in high}} (\text{SN74LS00})} \right|, \left| \frac{I_{\text{out low}} (\text{SN7400})}{I_{\text{in low}} (\text{SN74LS00})} \right| \right) \\ &= \min \left(\left| \frac{-4\text{E-}3\text{A}}{20\text{E-}6\text{A}} \right|, \left| \frac{16\text{E-}3\text{A}}{-4\text{E-}3\text{A}} \right| \right) \\ &= \min (20, 40) \\ &= \underline{\underline{20}} \end{aligned}$$

b) SN74LS00 drives SN7400

$$\begin{aligned} \text{Fanout} &= \min \left(\left| \frac{I_{\text{out high}} (\text{SN74LS00})}{I_{\text{in high}} (\text{SN7400})} \right|, \left| \frac{I_{\text{out low}} (\text{SN74LS00})}{I_{\text{in low}} (\text{SN7400})} \right| \right) \\ &= \min \left(\left| \frac{-4\text{E-}3\text{A}}{40\text{E-}6\text{A}} \right|, \left| \frac{8\text{E-}3\text{A}}{-1.6\text{E-}3\text{A}} \right| \right) \\ &= \min (10, 5) \\ &= \underline{\underline{5}} \end{aligned}$$

(4)

a) ON Semiconductor 74LS283

$$\text{Static Power} = P_S = V_{CC} \cdot I_{CC} = 5V \cdot 39E-3A = \underline{195E-3W} \quad (\text{Low})$$

$$P_S = V_{CC} \cdot I_{CC} = 5V \cdot 34E-3A = \underline{170E-3W} \quad (\text{High})$$

Dynamic Power is zero on TTL $\underline{P_D = 0W}$

$$\text{Total Power Dissipated} = P_S + P_D = P_T$$

$\frac{3}{4}$ of time = High $\frac{1}{4}$ of time = Low

$$\therefore P_T = \frac{3}{4}(170E-3W) + \frac{1}{4}(195E-3W) + 0W$$

$$P_T = \underline{\underline{.17625W}}$$

b) Philips 74F283

$$\text{For Low + High} \quad P_S = V_{CC} \cdot I_{CC} = 5V \cdot 55E-3A$$

$$P_D = 0 \quad (\text{TTL}) \quad P_S = \underline{\underline{.275W}}$$

$$P_T = \frac{3}{4}(.275W) + \frac{1}{4}(.275W) + 0$$

$$P_T = \underline{\underline{.275W}}$$

c) Philips 74HC283

$$P_S = V_{CC} \cdot I_{CC} = 5V \cdot 8 \mu A = \underline{40 \mu W} \text{ Watts}$$

(Low and High)

This IC has ~~dynamic~~ dynamic power dissipation

$$P_D = (C_{PD} + C_L) \cdot V_{CC}^2 \cdot \text{Frequency}$$

$$F = 100 \text{ kHz} \quad P_D = (88 \text{ pF} + 15 \text{ pF}) (25 \text{ V}^2) (100 \text{ kHz})$$

\downarrow
5V · 5V

$$P_D = \underline{.2575 \text{ mW}}$$

$$F = 1 \text{ MHz} \quad P_D = (88 \text{ pF} + 15 \text{ pF}) (25 \text{ V}^2) (1 \text{ MHz})$$
$$P_D = \underline{2.575 \text{ mW}}$$

$$f = 10 \text{ MHz} \quad P_D = (88 \text{ pF} + 15 \text{ pF}) (25 \text{ V}^2) (10 \text{ MHz})$$
$$P_D = \underline{.02575 \text{ W}}$$

$$P_T = P_S + P_D = (40 \mu W) + .2575 \text{ mW} = \underline{.2975 \text{ mW}}$$

(Frequency 100 kHz)

$$P_T = P_S + P_D = (40 \mu W) + 2.575 \text{ mW} = \underline{2.615 \text{ mW}}$$

(frequency 1 MHz)

$$P_T = P_S + P_D = (40 \mu W) + .02575 \text{ W} = \underline{.02579 \text{ W}}$$

⑤

$$C = 150 \text{ fF}$$

$$V_{CC} = 5 \text{ V}$$

$$F = 75 \text{ MHz}$$

a) Dynamic Power - $P_D = C \cdot V_{DD}^2 \cdot F$

$$= (150 \text{ E-15 F}) (5 \text{ V})^2 \cdot (75 \text{ E6 Hz})$$
$$= .28125 \text{ E-3 Watts}$$


b) Total Power Dissipated = 15% of 450,000 $\times P_D$

$$= (0.15)(450,000)(.28125 \text{ E-3 W})$$
$$\approx \underline{18.9 \text{ watts}}$$

Schmitt trigger is a comparator circuit that incorporates positive feedback.

- When input is higher than a certain threshold, the output is high
- When input is lower than a certain threshold, the output is low
- When input is between the two, the output retains value until the input changes sufficiently to trigger a change.
- Higher Noise Immunity than circuits with only one input threshold.

Symbol

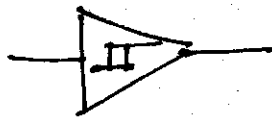

Schmitt trigger can be found useful for analog/digital systems that ~~require~~ require signal conditioning and discriminate noisy signals. The way it is used and its limitation is left to the imagination of the designer.